

A demonstration of cryogenic trans-impedance amplifier using fully-depleted silicon-on-insulator CMOS operational amplifier for far-infrared image sensor

Koichi Nagase(SOKENDAI/ISAS JAXA), Takehiko Wada, Hirokazu Ikeda (ISAS/JAXA), Yasuo Arai (KEK), Morifumi Ohno (AIST), Misaki Hanaoka, Hidehiro Kaneda, Shinki Oyabu, Yasuki Hattori, Sota Ukai (Nagoya Univ.), Toyoaki Suzuki (SRON), Kentaroh Watanabe (Univ. of Tokyo), Shunsuke Baba, Chihiro Kochi (Univ. of Tokyo/ISAS), Keita Yamamoto (SOKENDAI/ISAS)



Abstract

We are developing a low power cryogenic readout integrated circuit (ROIC) for large format far-infrared image sensor. As cryogenic electronics, we use fully-depleted silicon-on-insulator (FD-SOI) CMOS technology. FD-SOI MOSFETs show very stable static characteristics at 4.2 K. We report the trans-

impedance amplifier (TIA) circuit using FD-SOI CMOS OPAMP at cryogenic temperatures. In order to evaluate performance in measuring current for the TIA circuit, we combined the TIA circuit with the germanium blocked impurity band (Ge-BIB) detector as very small and calibrated current source.

Introduction

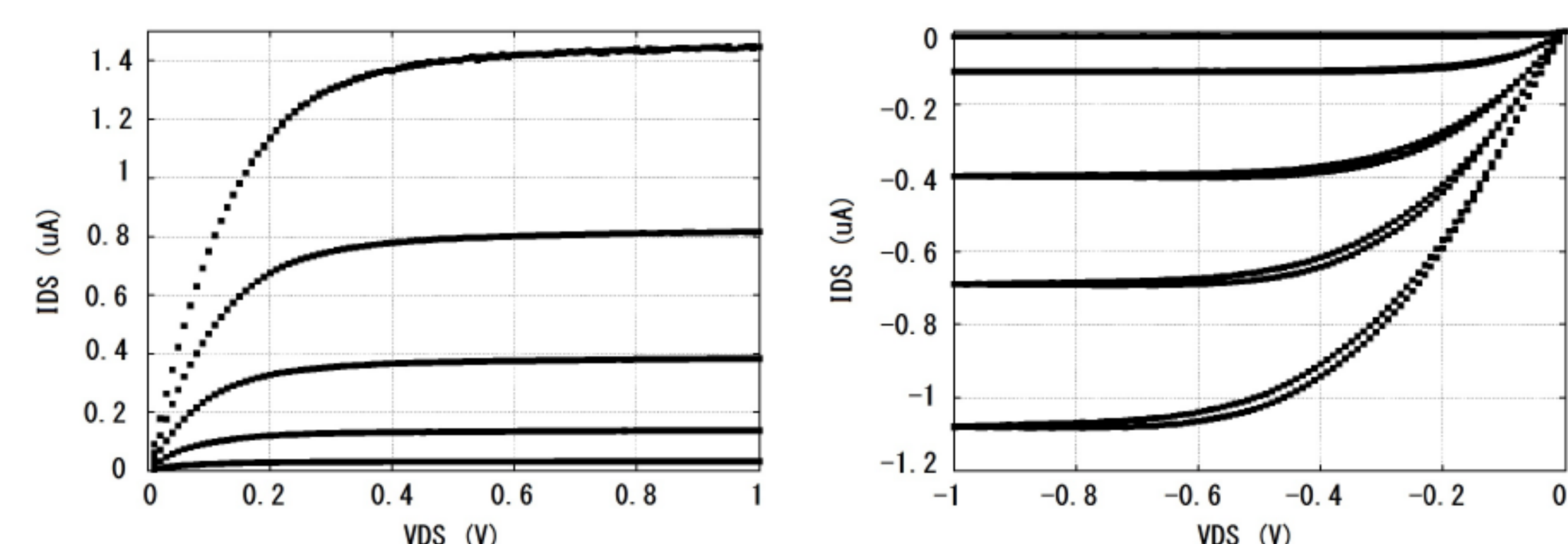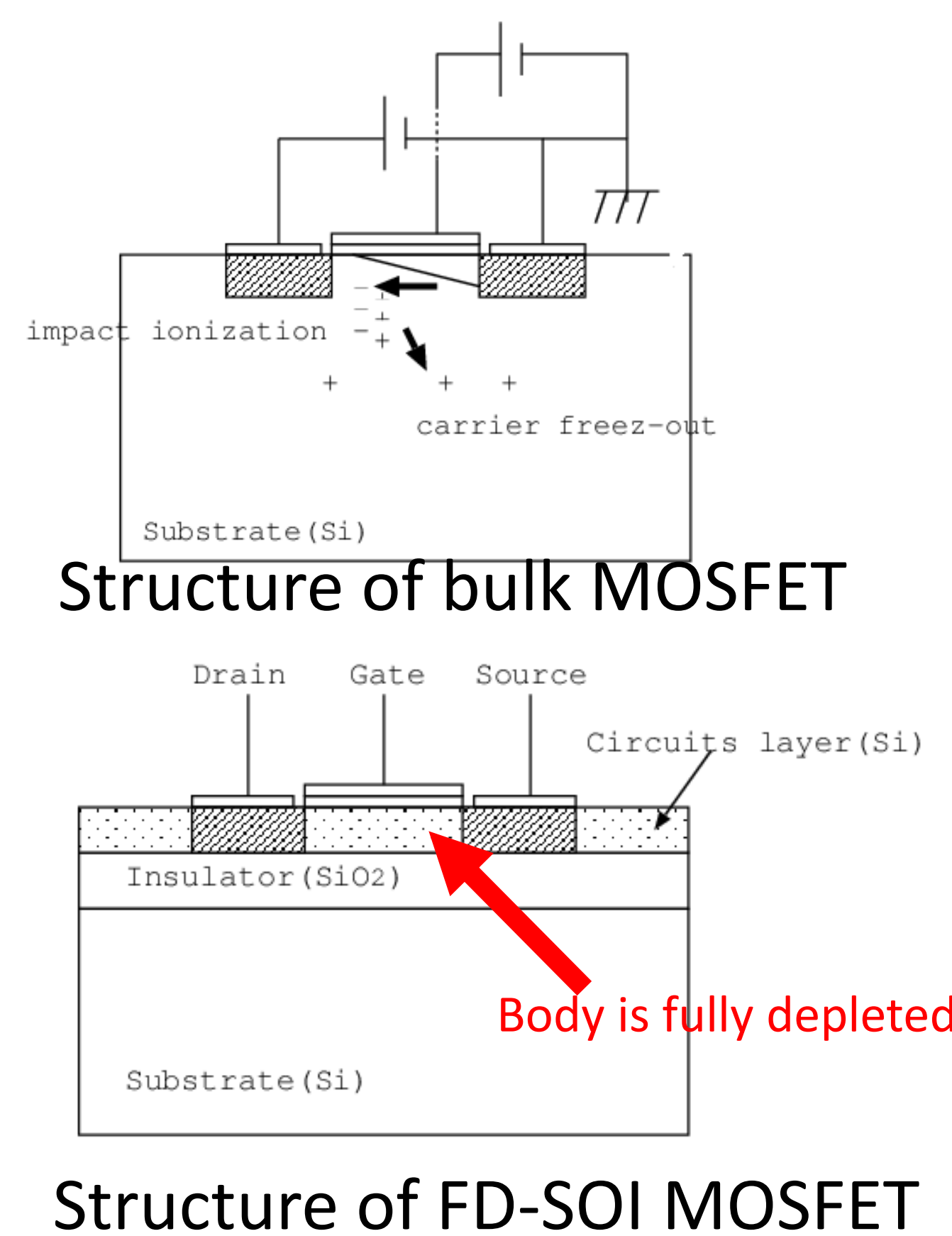
- Our goal is large format far-infrared image sensors Ge-BIB detectors + cryogenic electronics (See Hanaoka-san's poster and Wada-san's poster)
- Ge detector must be cooled down under 2K.
- Conventional bulk CMOS shows anomalous behavior at cryogenic temperatures
 - carrier freeze out
 - impact ionization
- Fully-depleted SOI CMOS shows very stable static characteristics under 4 K.



I-V curves of the FD-SOI MOSFETs
L:NMOS $V_g=0.9\text{ V}\leftrightarrow 1.1\text{ V}$
R:PMOS $V_g=-1.65\text{ V}\leftrightarrow -1.25\text{ V}$

Cryogenic readout electronics using FD-SOI CMOS

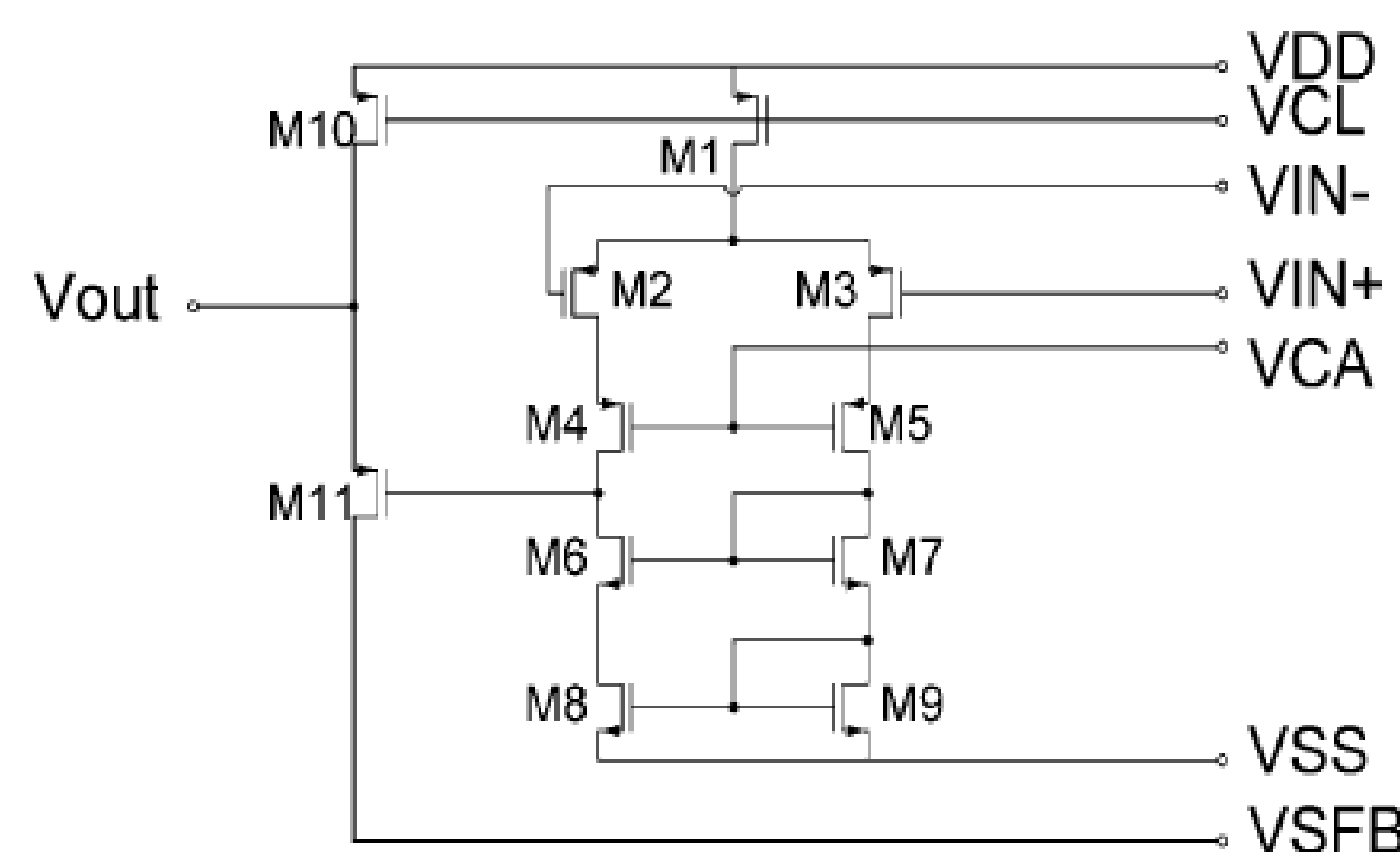- We successfully developed a cryogenic operational amplifier (OPAMP).
- We will design TIAs and CTIAs for measurements of ultra-low current (\sim fA).
- Low power consumption
 - large format a few mW for 32×32 pixels (1uW/pix)
 - low background no need to warm up
- High gain suitable for feedback circuits



Circuit diagram of our OPAMP

Performance of the FD-SOI CMOS amplifier at 4.2 K


	design	measurement
Open loop gain	> 1000	> 7000
Power consumption	1.1 μW	1.3 μW
Output Voltage swing	> 1V	1.3 V
Input referred noise at 1 Hz	14-20 $\mu\text{V}/\sqrt{\text{Hz}}$	19 $\mu\text{V}/\sqrt{\text{Hz}}$
Input offset voltage	0 mV	2mV
Variation of input offset voltage	0 mV	4.2 mV(1σ)

H. Nagata et al. IEICE Trans. Commun. Vol.E94-B, 2952, (2011)
T. Wada et al. J Low Temp Phys 167:602-608 (2012)


A demonstration of trans-impedance amplifier

Goals

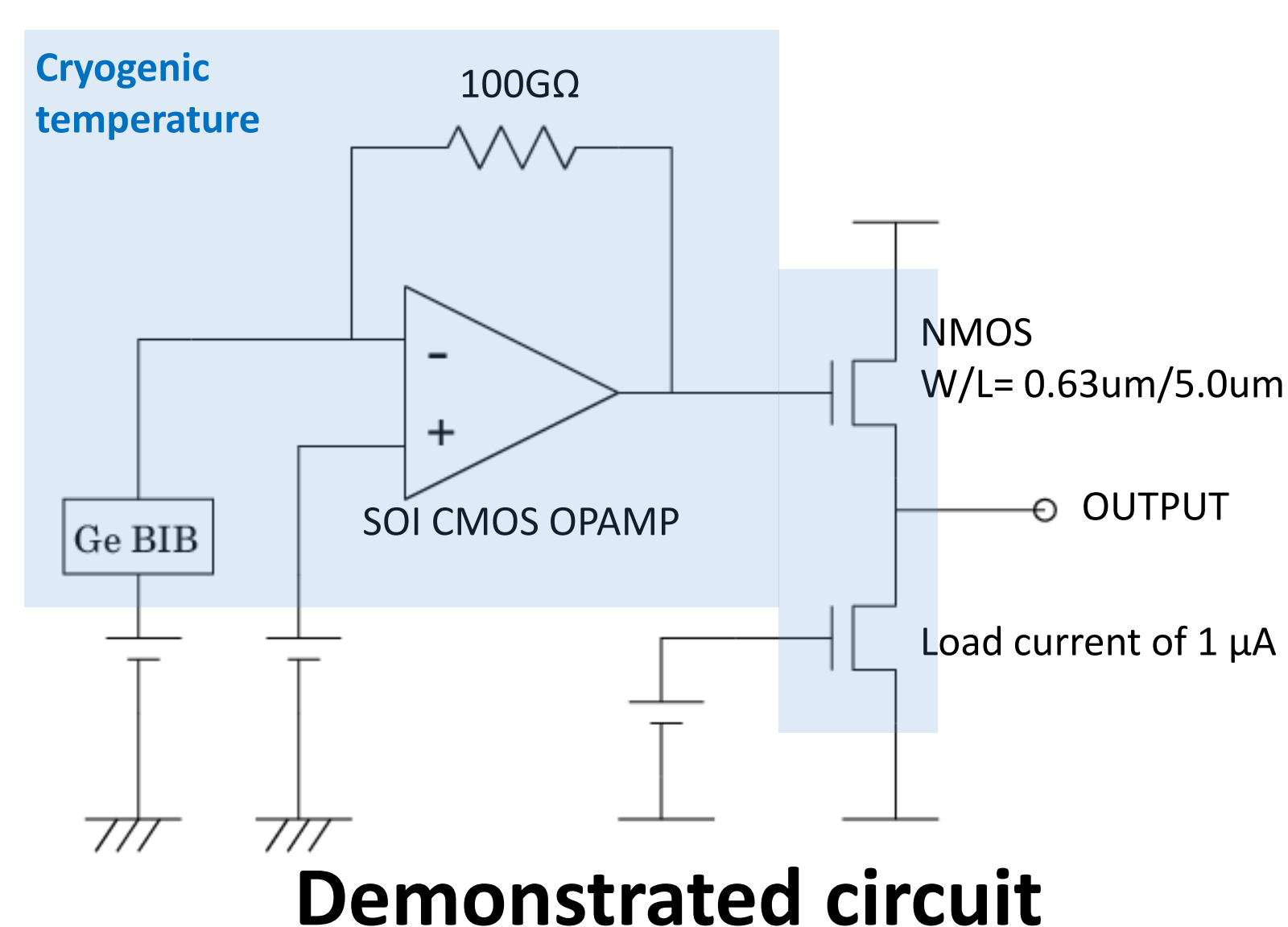- Operation under 4 K.
 - Measurement of ultra-low current(fA)
 - Ge-BIB detector as very low and calibrated current source. an intrinsic Ge + a Ge doped Ga of $1\text{E}+16/\text{cc}$
- H. Kaneda et al., JJAP 50, 066503 (2011)




Demonstrated circuit

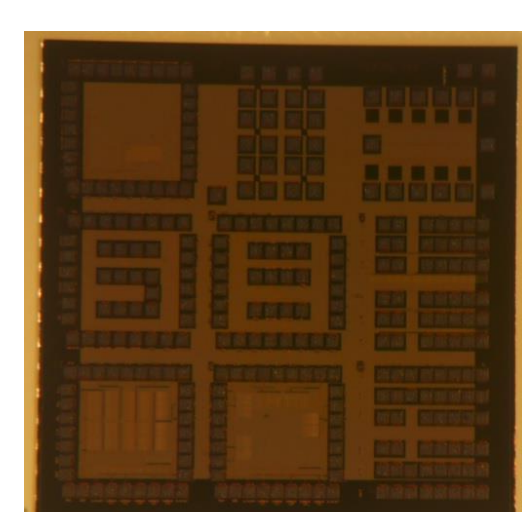

Test chip (2.9mm \times 2.9mm)
There is an OPAMP in this chip

Result

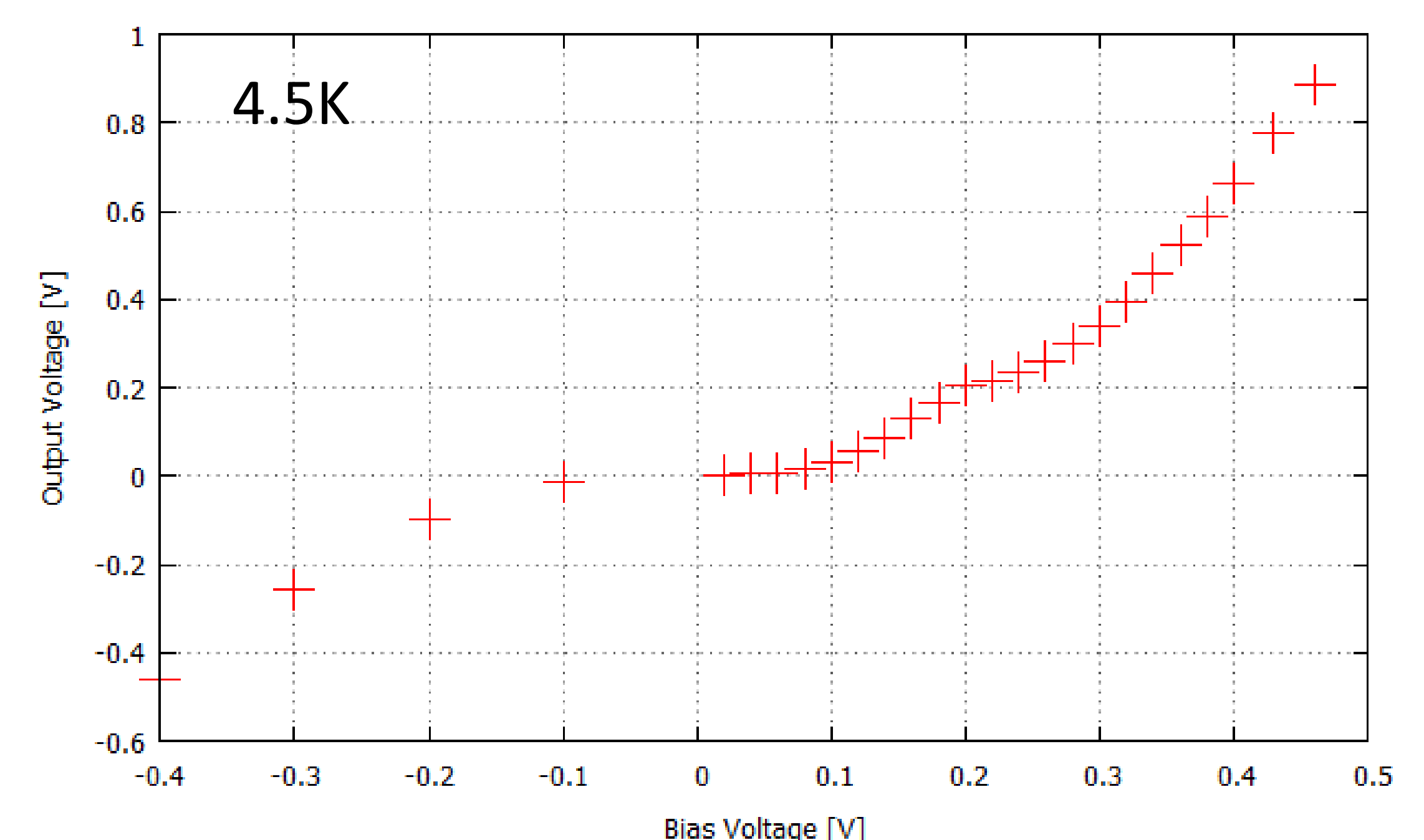

Output 32mV@Bias 0.1V \sim 300fA

Next step

We will measure dark current 1fA at 1.8 K. In addition, We will evaluate the image sensor of 5×5 pixels.

We measured dark current of Ge-BIB by using FD-SOI OPAMP at cryogenic temperatures.